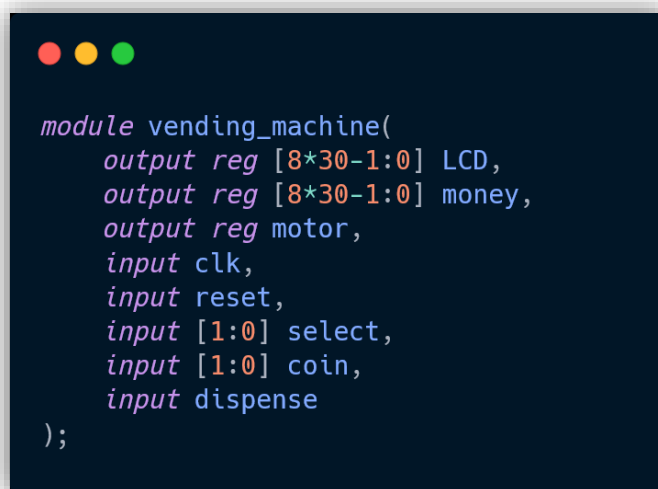


*"In the name of God"*

## Design and implementation of a digital vending machine controller using Verilog

By Zahra Azizi

This project aims to design a digital vending machine with 4 different products at different prices.



```
module vending_machine(  
    output reg [8*30-1:0] LCD,  
    output reg [8*30-1:0] money,  
    output reg motor,  
    input clk,  
    input reset,  
    input [1:0] select,  
    input [1:0] coin,  
    input dispense  
);
```

Fig. 1 - module

- Module definition

### Outputs

LCD = Displaying current states, an array of 30 \* 8 bits.

money = The amount to be returned or the amount that the user has entered.

motor = When the product is being dispensed, will become 1.

### Inputs

clk = Clock signal.

reset = When it becomes 1, the machine goes to idle state.



select = For choosing the product by the user.

coin = The amount of money that the user has entered.

dispense = When the product is being dispensed, the machine will go to the next state only if this becomes 1.

- Variables

- 1) current\_state
- 2) next\_state :This is defined based on the current state
- 3) product\_price: An array of 4 \* 8 bits.
- 4) product\_count
- 5) balance
- 6) change

```
reg [3:0] current_state;  
reg [3:0] next_state;  
  
reg [7:0] product_price [3:0];  
reg [7:0] product_count [3:0];  
  
integer balance;  
integer change;
```

Fig. 2 - Variables

- Assumptions

Assumptions for the products are as follows:

Name	Initial count	Price
Product 1	4	10c
Product 2	2	20c
Product 3	2	30c
Product 4	0	40c

```
initial begin  
    product_price[0] = 10;  
    product_price[1] = 20;  
    product_price[2] = 30;  
    product_price[3] = 40;  
  
    product_count[0] = 4;  
    product_count[1] = 2;  
    product_count[2] = 2;  
    product_count[3] = 0;  
end
```

Fig. 3 – Assumptions


- States

This machine includes 10 states:

1. **idle**: The machine doesn't do anything and is waiting for the user to choose a product. If the user chooses an out-of-stock product, it will go to the **out\_of\_stock** state.



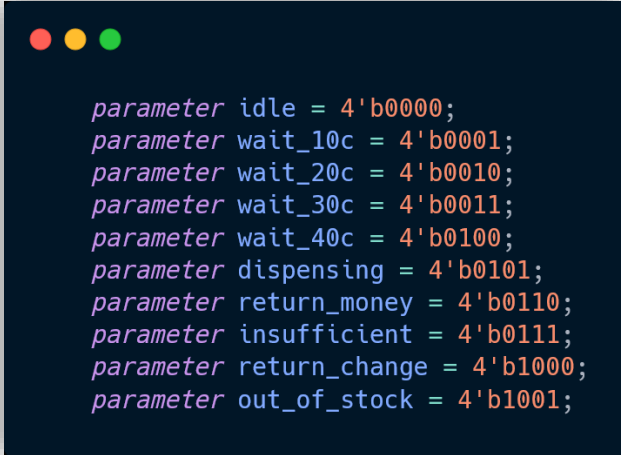2. **wait\_10c:** The user has picked the first product and the machine is waiting for coins to be inserted.
3. **wait\_20c:** The user has picked the second product and the machine is waiting for coins to be inserted.
4. **wait\_30c:** The user has picked the third product and the machine is waiting for coins to be inserted.
5. **wait\_40c:** The user has picked the fourth product and the machine is waiting for coins to be inserted.
6. **dispensing:** The machine is dispensing the product. This state will end when dispense becomes 1. After this state, the number of the selected product is decreased by one.
7. **return\_money:** If there isn't enough money, the whole money will be returned.
8. **insufficient:** It means the money is not enough and it will go to the **return\_money** state.
9. **return\_change**
10. **out\_of\_stock**



```
parameter idle = 4'b0000;  
parameter wait_10c = 4'b0001;  
parameter wait_20c = 4'b0010;  
parameter wait_30c = 4'b0011;  
parameter wait_40c = 4'b0100;  
parameter dispensing = 4'b0101;  
parameter return_money = 4'b0110;  
parameter insufficient = 4'b0111;  
parameter return_change = 4'b1000;  
parameter out_of_stock = 4'b1001;
```

Fig. 4 - states

```

always @(posedge clk or posedge reset) begin
    if (reset) current_state <= idle;

    else begin
        case (current_state)
            default: current_state <= idle;
            idle: begin
                if (product_count[select] > 0)
                    current_state <= next_state;
                else
                    current_state <= out_of_stock;
            end
            wait_10c, wait_20c, wait_30c, wait_40c, return_money, out_of_stock,
            insufficient, return_change: current_state <= next_state;
            dispensing: begin
                if (dispense == 1) begin
                    product_count[select] = product_count[select] - 1;
                    current_state <= next_state;
                end
                else
                    current_state <= dispensing;
            end
        endcase
    end
end

```

Fig. 5 – general state transition

- State transitions

State transitions are shown in the below diagram:

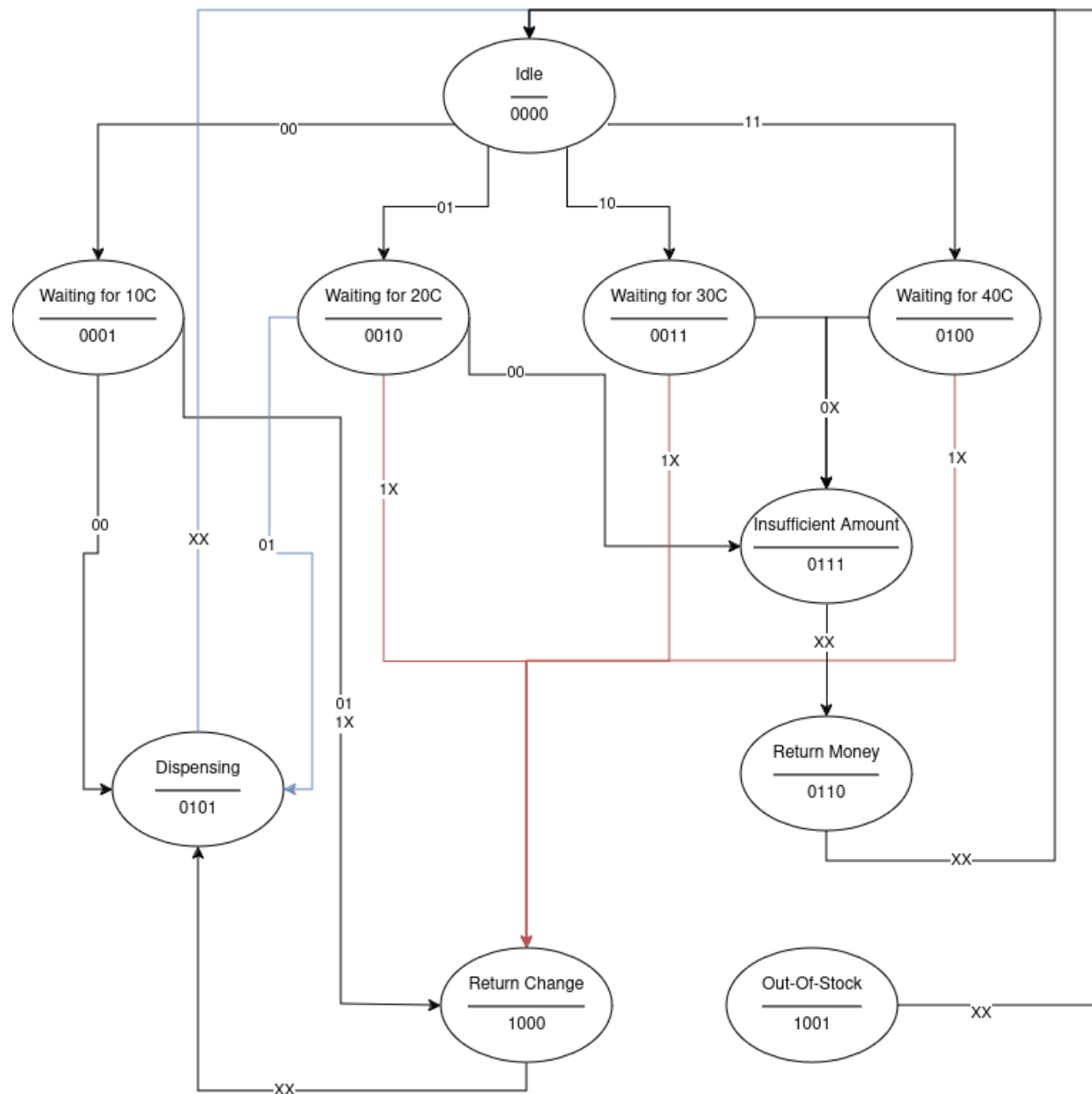


Fig. 6 –State diagram

```

always @(current_state or select or coin or dispense) begin
    case(current_state)
        default: next_state = idle;
        idle: begin
            next_state = (select == 2'b00) ? wait_10c :
                (select == 2'b01) ? wait_20c :
                (select == 2'b10) ? wait_30c :
                (select == 2'b11) ? wait_40c : idle;
        end
        wait_10c: case(coin)
            2'b00: next_state = dispensing;
            2'b01: next_state = return_change;
            2'b10, 2'b11: next_state = return_change;
        endcase
        wait_20c: case(coin)
            2'b00: next_state = insufficient;
            2'b01: next_state = dispensing;
            2'b10, 2'b11: next_state = return_change;
        endcase
        wait_30c, wait_40c: case(coin)
            2'b00: next_state = insufficient;
            2'b01: next_state = insufficient;
            2'b10, 2'b11: next_state = return_change;
        endcase
        return_change: next_state = dispensing;
        dispensing: next_state = ((dispense == 1) ? idle : dispensing);
        insufficient: next_state = return_money;
        return_money: next_state = idle;
        out_of_stock: next_state = idle;
    endcase
end

```

Fig. 7 – state transitions

The machine starts at an idle state and according to the user's choice, it will go to one of the wait\_xxc states. For instance, if the user chooses 01, it will go to wait\_20c. If there wasn't any product left, it would go to an out-of-stock state without waiting for money, then it would go to an idle state.

After entering wait\_xxc, according to the money inserted, the next state is defined:

- If the money is sufficient, the next state is dispensing.
- if not, the next state is insufficient then return\_money.

- If the amount that the user has inserted is more than the price, the machine will return the change, and then it will dispense the product.

### • خروجی ها

Outputs are determined based on current states so the functionality of the machine is visible in testbench code.

```
always @(current_state) begin
    case (current_state)
        default: current_state <= idle;
        idle: begin
            LCD <= "idle";
            money <= "0c";
            motor <= 0;
        end
        wait_10c: begin
            LCD <= "waiting for 10c";
            money <= "0c";
            motor <= 0;
        end
        wait_20c: begin
            LCD <= "waiting for 20c";
            money <= "0c";
            motor <= 0;
        end
        wait_30c: begin
            LCD <= "waiting for 30c";
            money <= "0c";
            motor <= 0;
        end
        wait_40c: begin
            LCD <= "waiting for 40c";
            money <= "0c";
            motor <= 0;
        end
        return_change: begin
            LCD <= "returning change";
            begin
                balance = (coin == 2'b00) ? 10 :
                    (coin == 2'b01) ? 20 :
                    (coin == 2'b10) ? 50 :
                    (coin == 2'b11) ? 100 : 0;
            end
            change = balance - product_price[select];
            money <= {"change: ", (change == 10) ? "10c" :
                (change == 20) ? "20c" :
                (change == 30) ? "30c" :
                (change == 40) ? "40c" :
                (change == 60) ? "60c" :
                (change == 70) ? "70c" :
                (change == 80) ? "80c" :
                (change == 90) ? "90c" : "0c"};
            motor <= 0;
        end
    endcase
end
```

Fig 8 & 9 - outputs

```
return_money: begin
    LCD <= "returning money";
    money <= {"return amount: ", (coin == 2'b00) ? "10c" :
        (coin == 2'b01) ? "20c" :
        (coin == 2'b10) ? "50c" :
        (coin == 2'b11) ? "100c" : "0c"};
    motor <= 0;
end
insufficient: begin
    LCD <= "insufficient";
    begin
        balance = (coin == 2'b00) ? 10 :
            (coin == 2'b01) ? 20 :
            (coin == 2'b10) ? 50 :
            (coin == 2'b11) ? 100 : 0;
    end
    change = product_price[select] - balance;
    money <= {"needs: ", (change == 10) ? "10c" :
        (change == 20) ? "20c" :
        (change == 30) ? "30c" : "0c"};
    motor <= 0;
end
out_of_stock: begin
    LCD <= "out of stock";
    money <= "ERROR";
    motor <= 0;
end
dispensing: begin
    LCD <= "dispensing";
    money <= {"inserted amount: ", (product_price[select] == 10) ? "10c" :
        (product_price[select] == 20) ? "20c" :
        (product_price[select] == 30) ? "30c" :
        (product_price[select] == 40) ? "40c" : "0c"};
    motor <= 1;
end
endcase
end
```

- Testbench

To verify the machine, we need to test it. We will create an instance of it according to the inputs and the outputs. In 5 time units, the clock signal will change. There are 7 test scenarios. After each test, there is a delay of 10 time units so the changes are visible in the terminal output. Before the start of the tests, the machine is reset. Time unit is 1 second and precision is 1 millie second.

```
`timescale 1s/1ms

module vending_machine_tb();

    reg clk = 0;
    reg reset;
    reg [1:0] select;
    reg [1:0] coin;
    reg dispense;

    wire [8*30-1:0] LCD;
    wire [8*30-1:0] money;
    wire motor;

    vending_machine vm (
        .clk(clk),
        .reset(reset),
        .select(select),
        .coin(coin),
        .dispense(dispense),
        .LCD(LCD),
        .money(money),
        .motor(motor)
    );

    always begin
        #5 clk = ~clk;
    end
```

Fig. 10 – instantiation and clock signal



```

$dumpfile("test_vm.vcd");
$dumpvars(0, vending_machine_tb);

dispense = 0;
reset = 1;
#10;
$display("before tests\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);
reset = 0;

```

```

// Test 1: Select item 1 (price 10c) and insert 10c
$display("Test 1-----");
select = 2'b00;
#10;
$display("select p1\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);
coin = 2'b00;
#10;
$display("insert 10c\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);
#10;
$display("dispense cont.\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);
dispense = 1;
#10;
$display("finished\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);

```

```

// Test 2: Select item 2 (price 20c) and insert 20c
$display("Test 2-----");
select = 2'b01;
#10;
dispense = 0;
$display("select p2\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);
coin = 2'b01;
#10;
$display("insert 20c\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);
dispense = 1;
#10;
$display("finished\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);

```

Fig. 11-13 – Initializing and test 1 &amp; 2

```
// Test 3: Select item 3 (price 30c) and insert 20c (insufficient)
$display("Test 3-----");
select = 2'b10;
dispense = 0;
#10;
$display("select p3\t Time: %0d | LCD: %s | money: %s | Motor: %b",
    $time, LCD, money, motor);
coin = 2'b01;
#10;
$display("insert 20c\t Time: %0d | LCD: %s | money: %s | Motor: %b",
    $time, LCD, money, motor);
#10;
$display("return money\t Time: %0d | LCD: %s | money: %s | Motor: %b",
    $time, LCD, money, motor);
#10;
$display("finished\t Time: %0d | LCD: %s | money: %s | Motor: %b",
    $time, LCD, money, motor);

// Test 4: Select item 3 (price 30c) and insert 50c (return change)
$display("Test 4-----");
select = 2'b10;
#10;
$display("select p3\t Time: %0d | LCD: %s | money: %s | Motor: %b",
    $time, LCD, money, motor);
coin = 2'b10;
#10;
$display("insert 50c\t Time: %0d | LCD: %s | money: %s | Motor: %b",
    $time, LCD, money, motor);
dispense = 1;
#10;
$display("change returned\t Time: %0d | LCD: %s | money: %s | Motor: %b",
    $time, LCD, money, motor);
#10;
$display("finished\t Time: %0d | LCD: %s | money: %s | Motor: %b",
    $time, LCD, money, motor);

// Test 5: Select item 4 (out of stock)
$display("Test 5-----");
select = 2'b11;
dispense = 0;
#10;
$display("select p4\t Time: %0d | LCD: %s | money: %s | Motor: %b",
    $time, LCD, money, motor);
#10;
$display("finished\t Time: %0d | LCD: %s | money: %s | Motor: %b",
    $time, LCD, money, motor);
```

Fig. 14-16 – test 3-5

```

//Test 6: Select item 3 then reset
$display("Test 6-----");
select = 2'b10;
#10;
$display("select p3.\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);
reset = 1;
#10;
$display("after reset\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);
reset = 0;

```

```

// Test 7: Select item 2 until it is out of stock
$display("Test 7-----");
select = 2'b01;
#10;
dispense = 0;
$display("select p2\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);
coin = 2'b01;
#10;
$display("insert 20c\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);
dispense = 1;
#10;
$display("dispense fin.\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);

select = 2'b01;
#10;
dispense = 0;
$display("select p2\t Time: %0d | LCD: %s | money: %s | Motor: %b",
        $time, LCD, money, motor);

#100;
$display("Finish-----");
$finish;

```

Fig. 17-18 – test 6 &amp; 7

```

before tests      Time: 10 | LCD:                idle | money:                0c | Motor: 0
Test 1-----
select p1         Time: 20 | LCD:                waiting for 10c | money:                0c | Motor: 0
insert 10c        Time: 30 | LCD:                dispensing | money:                inserted amount: 10c | Motor: 1
dispense cont.   Time: 40 | LCD:                dispensing | money:                inserted amount: 10c | Motor: 1
finished         Time: 50 | LCD:                idle | money:                0c | Motor: 0
Test 2-----
select p2         Time: 60 | LCD:                waiting for 20c | money:                0c | Motor: 0
insert 20c        Time: 70 | LCD:                dispensing | money:                inserted amount: 20c | Motor: 1
finished         Time: 80 | LCD:                idle | money:                0c | Motor: 0
Test 3-----
select p3         Time: 90 | LCD:                waiting for 30c | money:                0c | Motor: 0
insert 20c        Time: 100 | LCD:               insufficient | money:                needs: 10c | Motor: 0
return money     Time: 110 | LCD:               returning money | money:                return amount: 20c | Motor: 0
finished         Time: 120 | LCD:                idle | money:                0c | Motor: 0
Test 4-----
select p3         Time: 130 | LCD:                waiting for 30c | money:                0c | Motor: 0
insert 50c        Time: 140 | LCD:               returning change | money:                change: 20c | Motor: 0
change returned  Time: 150 | LCD:                dispensing | money:                inserted amount: 30c | Motor: 1
finished         Time: 160 | LCD:                idle | money:                0c | Motor: 0
Test 5-----
select p4         Time: 170 | LCD:                out of stock | money:                ERROR | Motor: 0
finished         Time: 180 | LCD:                idle | money:                0c | Motor: 0
Test 6-----
select p3.        Time: 190 | LCD:                waiting for 30c | money:                0c | Motor: 0
after reset      Time: 200 | LCD:                idle | money:                0c | Motor: 0
Test 7-----
select p2         Time: 210 | LCD:                waiting for 20c | money:                0c | Motor: 0
insert 20c        Time: 220 | LCD:                dispensing | money:                inserted amount: 20c | Motor: 1
dispense fin.    Time: 230 | LCD:                idle | money:                0c | Motor: 0
select p2        Time: 240 | LCD:                out of stock | money:                ERROR | Motor: 0
Finish-----

```

Fig. 19 – terminal output

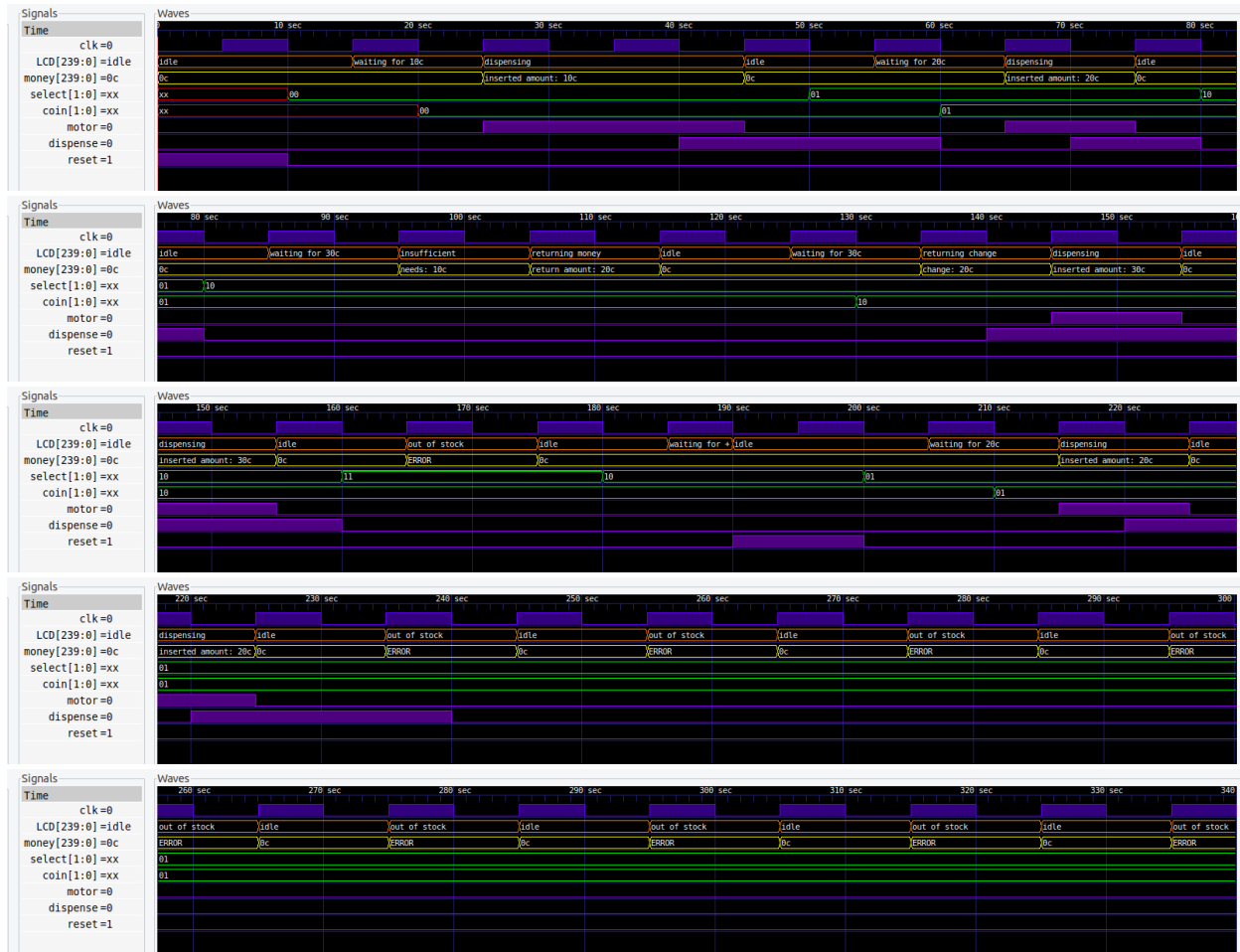


Fig. 20 -24 - waves

Compiled by Icarus Verilog and waves by gtkwave.

These files are attached to this report:

1. vending\_machine.v
2. vending\_machine\_tb.v
3. test\_vm.vcd
4. vending\_machine\_wave

\*\*\*